

Electronics HW4(a)

1.

(a) AND gate

(b) NOT gate

(c) OR gate

2. You could obtain these voltages experimentally using a series of switches arranged in parallel with a power supply. Switches that are set to ON would provide a high voltage input for logic gate while closed switches would provide 0V input for the OFF logic state.

(Any similar explanation or diagram is acceptable.)

3.

OR

INPUT		OUTPUT
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

AND

INPUT		OUTPUT
A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

NOT

INPUT	OUTPUT
0	1
1	0

4.

(a) At low temperatures, the voltage at X is 4V.

Working:

Resistance of resistor = R_1 (= 200 Ω)

Resistance of thermistor = R_2 (= 800 Ω)

Voltage across resistor = V_1

Voltage across thermistor = V_2

$$\frac{R_1}{R_2} = \frac{V_1}{V_2}$$

$$\frac{200\Omega}{800\Omega} = \frac{V_1}{V_2}$$

$$\frac{1}{4} = \frac{V_1}{V_2}$$

$$V_2 = 4V_1$$

$$V_1 + V_2 = 5V$$

$$V_1 + 4V_1 = 5V$$

$$5V_1 = 5V$$

$$V_1 = 1V$$

$$V_1 + V_2 = 5V$$

$$1V + V_2 = 5V$$

$$V_2 = 5V - 1V$$

$$V_2 = 4V$$

(b) This is logic level 1.

(c) Point Y is at logic level 0.

(d) The transistor is off.

(e) At the critical temperature, the voltage at point X is 0.45V.

Working:

Use same symbols as part (a) above

Resistance of resistor = R_1 (= 200Ω)

Resistance of thermistor = R_2 (= 20Ω)

Voltage across resistor = V_1

Voltage across thermistor = V_2

$$\begin{array}{l} \frac{R_1}{R_2} = \frac{V_1}{V_2} \\ \frac{200\Omega}{20\Omega} = \frac{V_1}{V_2} \\ 10 = \frac{V_1}{V_2} \\ V_1 = 10V_2 \end{array} \qquad \begin{array}{l} V_1 + V_2 = 5V \\ 10V_2 + V_2 = 5V \\ 11V_2 = 5V \\ V_2 = \frac{5V}{11} \\ V_2 = 0.45V \end{array}$$

(f) The logic level at point Y is 1.

(g) When the logic level at Y is 1, the voltage at the transistor base is high enough to turn the transistor on. The transistor then switches on the motor to open the windows.