

2008


Marks

24. Electrically heated gloves are used by skiers and climbers to provide extra warmth.



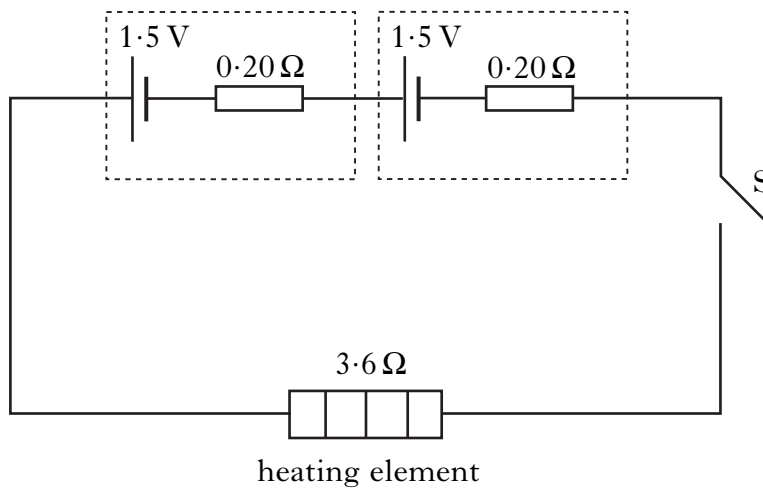- (a) Each glove has a heating element of resistance 3.6Ω .

Two cells, each of e.m.f. 1.5 V and internal resistance 0.20Ω , are used to operate the heating element.




Switch S is closed.

- (i) Determine the value of the total circuit resistance. 1
- (ii) Calculate the current in the heating element. 2
- (iii) Calculate the power output of the heating element. 2
- (b) When in use, the internal resistance of each cell gradually increases.
What effect, if any, does this have on the power output of the heating element?
Justify your answer. 2
- (7)**


[Turn over

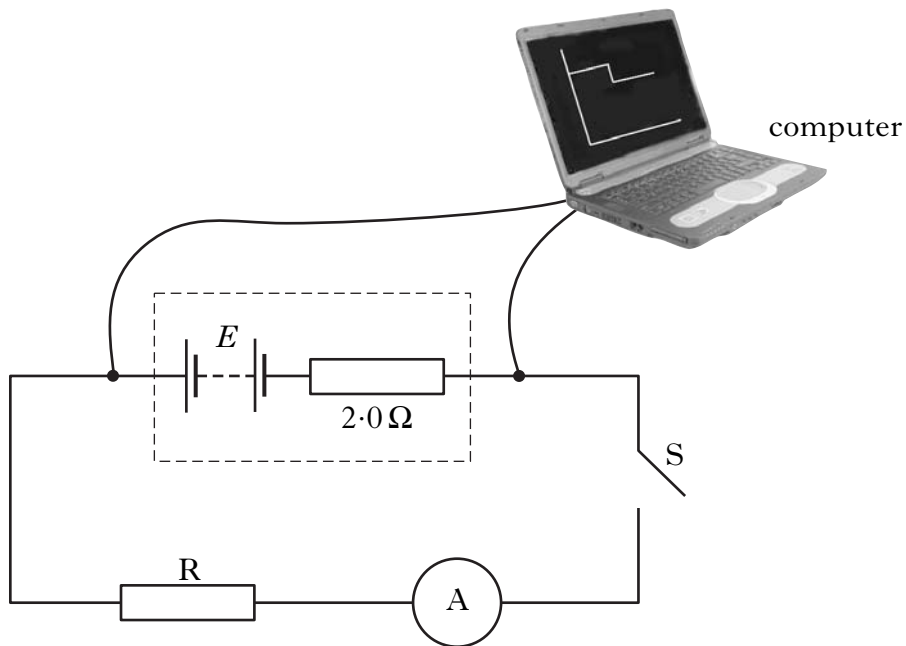25. A power supply of e.m.f. E and internal resistance $2.0\ \Omega$ is connected as shown.



The computer connected to the apparatus displays a graph of potential difference against time.

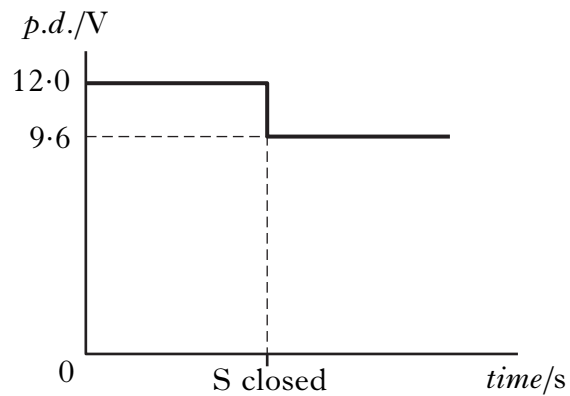
The graph shows the potential difference across the terminals of the power supply for a short time before and after switch S is closed.




- (a) State the e.m.f. of the power supply. 1
- (b) Calculate:
- (i) the reading on the ammeter after switch S is closed; 2
- (ii) the resistance of resistor R . 1

25. (continued)

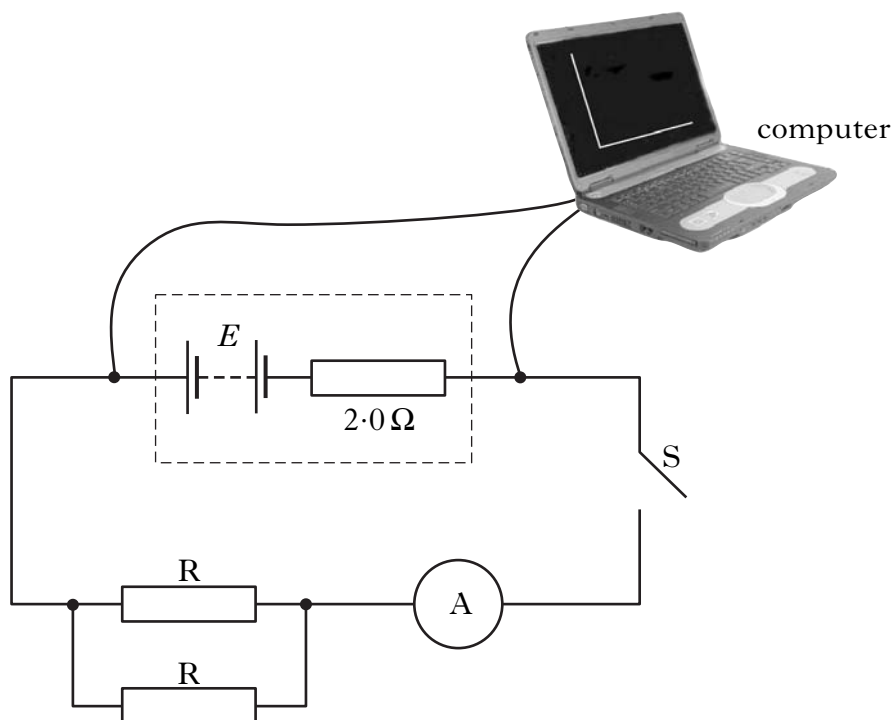- (c) Switch S is opened. A second identical resistor is now connected in parallel with R as shown.



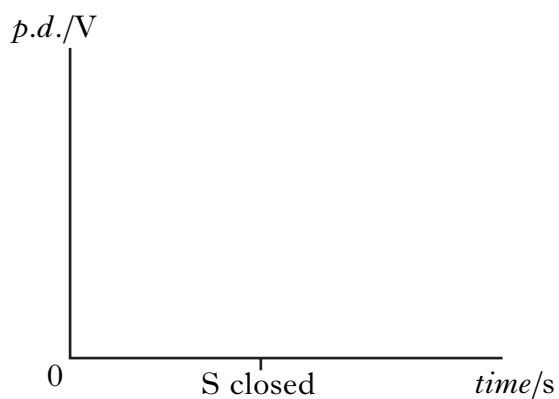The computer is again connected in order to display a graph of potential difference against time.



Copy and complete the new graph of potential difference against time showing the values of potential difference before and after switch S is closed.

2
(6)

[Turn over