

KU Revision Questions for Electricity & Energy Unit Assessment

mrmackenzie.co.uk





DO NOT WRITE IN THIS MARGIN Marks 29. (a) An electronic system consists of three parts. Complete the block diagram below. INPUT 1 (b) Some electronic devices are listed below. microphone switch motor loudspeaker LED lamp (i) Complete the table below by putting each device in the correct column. Input device Output device 3 (ii) What is the energy change in an LED? 1



WRITE IN THIS MARGIN

Marks

1

1

1

DO NOT

22. A "hands-free" system for a mobile phone has an earpiece and a microphone.



- (*a*) State the useful energy change that takes place in the:
 - (i) earpiece;
 - (ii) microphone.
- (b) State **one advantage** of using a mobile phone instead of a landline.

(c) Give **one** reason why it is difficult for a mobile phone to pick up signals in a steep-sided valley.



THIS MARGIN Marks In a car, a warning sounds if the lights are left on after the ignition switch is 31. turned off. The system has two inputs, one from the ignition switch and the other from the light switch. Х Ignition switch Output Light switch (a)Name logic gate X. 1 Complete the logic table for gate X. *(b)* Logic level from ignition switch Output logic level from the gate 0 1 1 *(c)* Some electronic devices are listed below. microphone buzzer LDR thermistor motor Select an appropriate output device for this system. 1

DO NOT WRITE IN



- Marks
- **33.** Lights in a shop window are connected to an electronic system which switches them on when it becomes dark. The lights can also be switched on by a master switch.



(a) A diagram for the electronic system is shown below.







25. A student's games console stops working. She builds the circuit below to test the fuse in the plug.

(a) The student touches the metal probes together and bulb Y lights.She connects the metal probes to the fuse from the games console. This time bulb Y does not light. What might be wrong with the fuse?

X is used to vary the brightness of bulb Y. What is component X?

1

The table shows information about the appliances.

Appliance	<i>Voltage in</i> volts	Power in watts	Current in amperes
Microwave oven	230	690	3
Toaster	230	1150	5
Kettle	230	2070	

(a) Show by calculation that the current in the kettle is 9 amperes when operating.

You **must** show your working.

DO NOT WRITE IN THIS MARGIN Marks 24. (continued) The adaptor is fitted with a 13 ampere fuse. *(b)* (i) Which **two** appliances must **not** be switched on at the same time? 1 (ii) Explain your answer. 1 [Turn over

DO NOT WRITE IN THIS MARGIN Marks 31. (continued) (c) After the experiment, the student plotted the following graph. Resistance in ohms > 0 Temperature in degrees Celsius (i) Was the thermistor working correctly? 1 (ii) Explain your answer. 1

23. (a) A technician for a lamp company is investigating the properties of a lamp at different voltages.

For different voltages the technician measures the current in the lamp. The graph of her results is shown below.

(i) What is the value of mains voltage?

DO NOT WRITE IN THIS MARGIN Marks (a) (continued) 23. (ii) What is the current in the lamp when it is being operated at mains voltage? 1 (iii) Calculate the resistance of the bulb at mains voltage. 2 (b) The bulb is now operated at a lower voltage than mains voltage. (i) Will the resistance of the bulb be bigger, smaller or the same as your answer in (*a*)(iii)? 1 (ii) Explain your answer. 1 [Turn over

Marks

30. A car alarm system has two sensors.

One sensor activates if someone smashes a window. The second sensor activates if someone tries to move the car. Each sensor gives a high output when activated.

(a) The two sensors are connected to a logic gate as shown.

Complete the table to show the output from the logic gate.

Logic level of window sensor	Logic level of movement sensor	Output logic level of gate
0	0	
0	1	
1	0	
1	1	

